

## Summary Direct Current

### Revise last year's chapter on DC

Ohm's law:  $V = IR$ ;  $V \rightarrow$  voltage,  $I \rightarrow$  current,  $R \rightarrow$  resistance

Resistors in series share same current:  $R_{tot} = R_1 + R_2$

Resistors in parallel share same voltage:  $\frac{1}{R_{tot}} = \frac{1}{R_1} + \frac{1}{R_2}$

Current is Charge per Second: in units:  $A = Cs^{-1}$

Voltage is Work per Charge: in units:  $V = JC^{-1}$

Electric Power is Volt x Current in units:  $W = VA$  or  $Cs^{-1} \times JC^{-1} = Js^{-1}$  or Work per second

Electric Energy is Electric Power x Time in units:  $J = Ws$  (household unit is kWh)

### Geometry of Resistance


$$R = \frac{\rho L}{A};$$

$R$  is resistance of a wire,


$\rho$  is resistivity,  $L$  is length,  $A$  is area of cross section
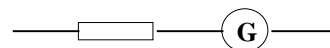
### Multimeters

- Voltmeter is Galvanometer in series with (large) resistor. This leaves low voltage for the galvanometer.



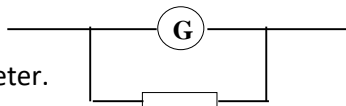
- Ammeter is Galvanometer in parallel with (small) resistor. This shunts off most current and leaves little current for the galvanometer.



### Kirchhoff's laws


- At junction in circuit:

$$\Sigma i = 0$$

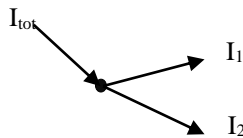

- In loop in circuit:

$$\Sigma V = 0$$

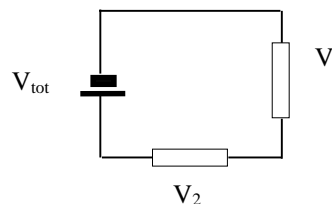

See Exercise 2 p 174 as typical example of applying these laws.

### EMF, Internal Resistance

A Power Supply has an internal resistance  $r$ . This means that there is a difference between open circuit voltage of the supply and the supply voltage when connected to a circuit.

The voltage drop depends on the current drawn:  $V_{drop} = Ir$

Hence  $V_{(out)} = E - Ir$